

Electricity



Electric Current : The rate of flow of charge is called electric current.

- S.I Unit \rightarrow Ampere (A)

- The electric current is measured by Ammeter.

- $i = \frac{Q}{t}$, i = current, Q = charge (in Coulomb)

Electric Potential : The work done in bringing a unit positive charge from infinity to a point inside the electric field is defined as electric potential at that point.

Electric Potential Difference : The amount of work done in bringing a unit positive charge from one point to another in an electric field is called potential difference between these two points.

- S.I Unit \rightarrow Volts (V)

- The potential difference is measured by Voltmeter.

- $V = \frac{W}{Q}$

★ ★ ★

Ohm's Law :
(V-Imp)

If physical conditions like temperature remain constant, the potential difference across the ends of a conductor is directly proportional to the current flowing through it.

- $V = iR$ \rightarrow Resistance

Resistance (R) : The opposition or obstruction offered by a conductor to the flow of electrons is called electric resistance.

- S.I Unit \rightarrow Ohm (Ω)

- ~~Object~~ A conductor is said to have 1 Ω resistance if a current of 1A flows through it at a potential difference of 1V.

Electricity - Formula Sheet



(i) Electric current (i)

$$i = \frac{Q}{t}$$

$Q \rightarrow$ charge and $t \rightarrow$ time

(ii) Potential Difference (V_d)

$$V_d = \frac{W}{Q}$$

$W \rightarrow$ work done and $Q \rightarrow$ charge

(iii) Ohm's law

$$V = iR$$

$R \rightarrow$ Resistance

(iv) Resistance (R)

$$R = \frac{\rho l}{a}$$

$\rho \rightarrow$ Resistivity, $l \rightarrow$ length of conductor, $A \rightarrow$ area of c/s

(v) Combination of Resistors

$$\text{Series: } R_s = R_1 + R_2 + R_3 + \dots$$

$$\text{Parallel: } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

(vi) Heat and Power

$$H = i^2 R t = V i t = \frac{V^2}{R} \times t$$

$$P = i^2 R = V i = \frac{V^2}{R}$$

Electric Power : The electric power of a conductor is given by the expressions

$$P = VI = i^2 R = \frac{V^2}{R}$$

- Unit of electric power is Watt (W).
- One Watt is the power, when a current of 1A flows through a conductor at a potential difference of 1V.

Commercial Unit of Energy: The commercial unit of energy is kilowatt-hour (kWh).

$$1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$$



Electricity Diagrams



Electric cell



Battery




Switch open



Switch Closed



Wire joint

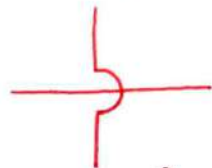

Wire crossing without joint



Electric bulb



Resistor



Rheostat




Ammeter



Voltmeter



Series Combination

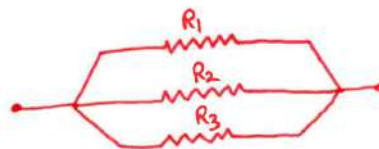

Parallel Combination